

CSE 232 SPRING 2020
HOMEWORK 3

NEVZAT SEFEROGLU
171044024

CSE 232 SPRING 2020

HOMEWORK 3

Due Date May 8, Friday


1. Compute the clock period for the following clock frequencies.

- a. 50 kHz (early computers)
- b. 300 MHz (Sony Playstation 2 processor)
- c. 3.4 GHz (Intel Pentium 4 processor)
- d. 10 GHz (PCs of the early 2010s)
- e. 1 THz (1 terahertz) (PCs of the future?)


$$\text{clock period} = 1 / (\text{clock frequency})$$

- a -) $(1 / 50.000) \text{ s} = 0.00002 \text{ s} = 20000 \text{ ns}$
- b -) $(1 / (300 * 10^6)) \text{ s} = (3.33 * 10^{-9}) \text{ s} = 3.33 \text{ ns}$
- c -) $(1 / (3.4 * 10^9)) \text{ s} = 0.294 \text{ ns}$
- d -) $(1 / (10 * 10^9)) \text{ s} = 0.1 \text{ ns}$
- e -) $(1 / (1 * 10^{12})) \text{ s} = 0.001 \text{ ns}$

 2. Trace the behavior of a level-sensitive SR latch for the input pattern in below figure. Assume S1, R1, and Q are initially 0. Complete the timing diagram for S1, R1 and Q, assuming logic gates have a tiny but nonzero delay.



 3. Compare the behavior of D latch and D flip-flop devices by completing the timing diagram adding Q (latch) and Q (flip-flop) in below figure. Provide a brief explanation of the behavior of each device. Assume each device initially stores a 0.




4. FSMs with the following numbers of states, indicate the smallest possible number of bits for a state register representing those states:
- a. 4 b. 8 c. 9 d. 23 e. 900

Encoding : Assigning unique binary number (encoding) to each state. Usually using fewest bits, assigning encoding to each state by counting **in binary**.


- a -) $\text{CEIL} (\log_2(4)) = 2$ bits
b -) $\text{CEIL} (\log_2(8)) = 3$ bits
c -) $\text{CEIL} (\log_2(9)) = 4$ bits
d -) $\text{CEIL} (\log_2(23)) = 5$ bits
e -) $\text{CEIL} (\log_2(900)) = 10$ bits

 5. If an FSM has N states, what is the maximum number of possible transitions that could exist in the FSM? Assume that no pair of states has more than one transition in the same direction, and that no state has a transition point back to itself. Assuming there are a large number of inputs, meaning the number of transitions is not limited by the number of inputs? Hint: try for small N, and then generalize.



For $N = 4$, there are 4×3 different transitions can be occurred. Therefore, if we have N number of states, each state matches $N - 1$ unique state other than itself. According to given rule, there should be $N * (N - 1)$ transitions as a maximum number of possible transitions.

 6. Draw a state diagram for an FSM with no inputs and three outputs x, y, and z. xyz should always exhibit the following sequence: 000, 001, 010, 100, repeat. The output should change only on a rising clock edge. Make 000 the initial state. Using the process for designing a controller, convert the FSM to a controller, stopping once you have created the truth table and derive the Boolean expressions.



| INPUTS | | OUTPUTS | | | | |
|--------|----|---------|----|---|---|---|
| S1 | S0 | n1 | n0 | x | y | z |
| 0 | 0 | 0 | 1 | 0 | 0 | 0 |
| 0 | 1 | 1 | 0 | 0 | 0 | 1 |
| 1 | 0 | 1 | 1 | 0 | 1 | 0 |
| 1 | 1 | 0 | 0 | 1 | 0 | 0 |

$$x = S1S0, y = S1S0', z = S1'S0$$

$$n1 = S1'S0 + S1S0', n0 = S1'S0' + S1 + S0'$$

-
- ```

graph TD
 Time1((Time1
S1 = 0
S0 = 0)) -- B' --> Time2((Time2
S1 = 0
S0 = 0))
 Time2 -- B --> Alarm1((Alarm1
S1 = 0
S0 = 1))
 Alarm1 -- B' --> Alarm2((Alarm2
S1 = 0
S0 = 1))
 Alarm2 -- B --> Stopwatch1((Stopwatch1
S1 = 1
S0 = 0))
 Stopwatch1 -- B' --> Stopwatch2((Stopwatch2
S1 = 1
S0 = 0))
 Stopwatch2 -- B --> Date1((Date1
S1 = 1
S0 = 1))
 Date1 -- B' --> Date2((Date2
S1 = 1
S0 = 1))
 Date2 -- B --> Time1
 Time1 -- B --> Time1
 Time2 -- B' --> Time2
 Alarm1 -- B --> Alarm1
 Alarm2 -- B' --> Alarm2
 Stopwatch1 -- B --> Stopwatch1
 Stopwatch2 -- B' --> Stopwatch2
 Date1 -- B --> Date1
 Date2 -- B' --> Date2

```

**n2 , n1 , n0** are outputs of combinational circuit, inputs of state register.

**S1** , **S0** are general outputs.

[illegible]

**Boolean equations for constructing conventional circuit :**

$$\mathbf{n2} = K2^{\sim} K1 K0 B^{\sim} + K2 K1^{\sim} K0^{\sim} B^{\sim} + K2 K1^{\sim} K0^{\sim} B + K2 K1^{\sim} K0 B^{\sim} + K2 K1^{\sim} K0 B + K2 K1 K0^{\sim} B^{\sim} + K2 K1 K0^{\sim} B + K2 K1 K0 B$$

$$\mathbf{n1} = K2^{\sim} K1^{\sim} K0 B^{\sim} + K2^{\sim} K1 K0^{\sim} B^{\sim} + K2^{\sim} K1 K0^{\sim} B + K2^{\sim} K1 K0 B + K2 K1^{\sim} K0 B^{\sim} + K2 K1 K0^{\sim} B^{\sim} + K2 K1 K0^{\sim} B + K2 K1 K0 B$$

$$\mathbf{n0} = K2^{\sim} K1^{\sim} K0^{\sim} B + K2^{\sim} K1^{\sim} K0 B + K2^{\sim} K1 K0^{\sim} B + K2^{\sim} K1 K0 B + K2 K1^{\sim} K0^{\sim} B + K2 K1^{\sim} K0 B + K2 K1 K0^{\sim} B + K2 K1 K0 B$$